MULTIMEDIA UNIVERSITY

STUDENT ID NO

MULTIMEDIA UNIVERSITY

FINAL EXAMINATION

TRIMESTER 2, 2016/2017

EMG4076 – ELECTROMAGNETIC INTERFERENCE

(TE)

9 MARCH 2017
2.30 P.M. – 4.30 P.M.
(2 Hours)

INSTRUCTION TO STUDENT

1. This Question paper consists of 5 pages including cover page with 4 Questions only.

2. Attempt all **FOUR** questions. All questions carry equal marks and the distribution of the marks for each question is given.

3. Please write all your answers in the answer Booklet provided.

Question 1

(a) Consider three parallel wires, two are the signal leads (lead-1 and lead-2) and the third is a common signal-return lead (lead-G). The circuit of Figure Q1 represents the capacitive and the inductive couplings between the circuits. Consider resistive source and termination impedances only: R_{1S}, R_{1L}, R_{2S} and R_{2L}.

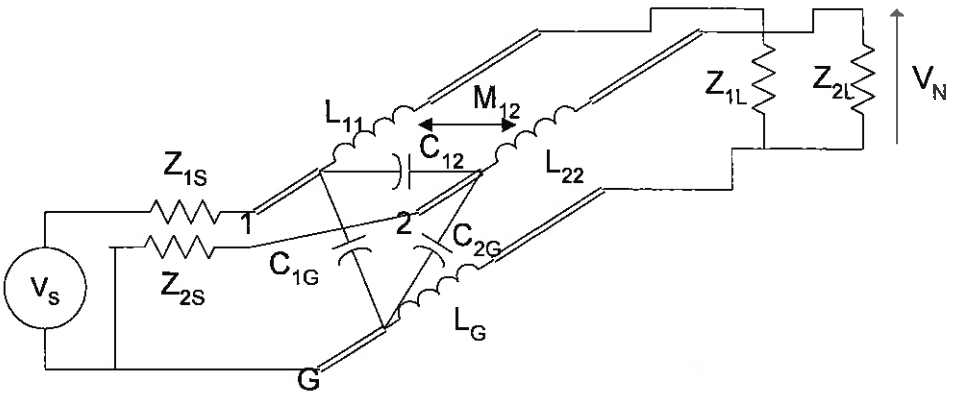

Figure Q1

(i) Draw the equivalent circuit due to capacitive coupling.

[4 marks]

(ii) By analyzing the circuit in (a)(i), derive the noise voltage, V_N due to capacitive coupling.

[11 marks]

(iii) Derive an approximate expression for V_N at low frequency, mid-frequency and high frequency.

[6 marks]

(iv) Sketch the frequency response for the noise voltage due to capacitive coupling.

[4 marks]

Continued...

Question 2

(a) Partitioning of a printed circuit board (PCB) layout is necessary to reduce the interference among the components and different types of circuit on the PCB. Describe five (5) steps in PCB layout and portioning process.

[10 marks]

(b) The circuit in Figure Q2.1 represents the connection of a Class-B Power Amplifier (PA) to its signal source. Impedance Z_L represents the speaker load, while Z_1, Z_2 and Z_3 represent the impedance of interconnecting wires.

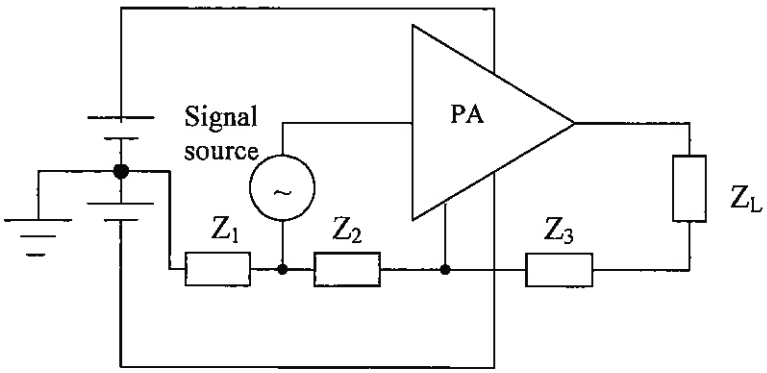

Figure Q2.1

(i) Explain how common impedance coupling can cause the power amplifier (PA) to oscillate.

[4 marks]

(ii) Propose a better schematic of connection to overcome the oscillation problem.

[5 marks]

(c) Explain the electrostatic discharge (ESD) in an electronic circuit. State four (4) ESD coupling mechanisms.

[6 marks]

Continued...

Question 3

(a) Signal from a source can be coupled to distant device by means of radiated emission. State three (3) design techniques to minimize radiation due to:

(i) Current loop

[3 marks]

(ii) Electric dipole

[3 marks]

(b) An electronic device operating at 100MHz is to be installed in a shielded enclosure made of an annealed copper. The conductivity and relative permeability of the shield material are 5.82×10^7 S/m and 1, respectively. For a perfectly shielded enclosure, determine the following:

(i) The thickness of the shield to provide an absorption loss of 90 dB.

[3 marks]

[Hint: $\delta = \sqrt{\frac{2}{\mu\omega\sigma}}$, $\mu_0 = 4\pi \times 10^{-7}\, H/m$, $\varepsilon_0 = 8.854 \times 10^{-12}\, F/m$]

(ii) The reflection loss and the shielding effectiveness of this enclosure in dB, assuming that multiple reflection loss is negligible.

[3 marks]

[Hint: $R = 20\log(30\pi\sqrt{\frac{\sigma}{\mu\omega}})$ dB]

(iii) A stainless steel with a relative conductivity of 0.01 and relative permeability of 200 is used as the material for the shielded enclosure. By using the same thickness in (b)(i), calculate the absorption loss and the shielding effectiveness of this material.

[5 marks]

(iv) Conclude your observation about the shielding effectiveness for both materials.

[2 marks]

(c) Propose three (3) treatments on the slots in cabinet shielding in order to reduce the electromagnetic interference (EMI) leakage.

[6 marks]

Continued...

Question 4

(a) Electromagnetic compatibility (EMC) regulation is very important to control the level of radiated and conducted emission. State four (4) types of EMC test defined by the European standard.

[4 marks]

(b) Radiated susceptibility is defined as the ability of equipment to function as desired in the presence of radiated interference.

(i) Using suitable diagram, explain the test setup for radiated susceptibility test.

[9 marks]

(ii) Briefly explain four (4) degradation grades in evaluating the performance of the equipment-under-test in an electromagnetic interference susceptibility test.

[8 marks]

(c) The regulatory limits of radiated emission are usually based on quasi-peak values. Contrast the difference between a quasi-peak detector and a peak detector.

[4 marks]

End of Page